

Write up- Lab6
Simranpreet Kaur
May 20, 2022
Lab Section C

Objective:

The objective of this lab was to design a state machine for a game where we would be using signals to count the number of turkeys crossing the sensors which are simulated by our buttons. The sensors are high by default but when a turkey crosses either or both sensors, the output becomes low. If the turkey crosses right to left, we increment the count by one. If the turkey crosses left to right, we decrement the count by 1, and if the turkey does not cross both sensors all the way, the counter stays the same.

Methods and Design:


In order to complete this lab, I imported many old modules from previous labs and also built new modules which include:

- State machine: the state machine takes the sensor inputs and sends outputs to control the turkey and time counters. These outputs will be displayed on the 7 segment display
- Turkey Counter: 8-bit counter that counts up and down
- Time Counter: 8-bit counter that keeps track of time using qsec

Top Level:

In my top level, I called all the modules that needed to be connected and made wires for all their outputs. In my top level, I also included the anode logic where I had to make sure that the leftmost anode (an[3]) only displays the time counter, an[2] only displays the negative sign if needed, and an[1] and an[0] display the turkey counter. My LED's 9 and 15 were set to ~btnR and ~btnL respectively. The logic for negatives using muxes, and the logic for implementing two's complement were also written in my top.

Top Level Diagram:

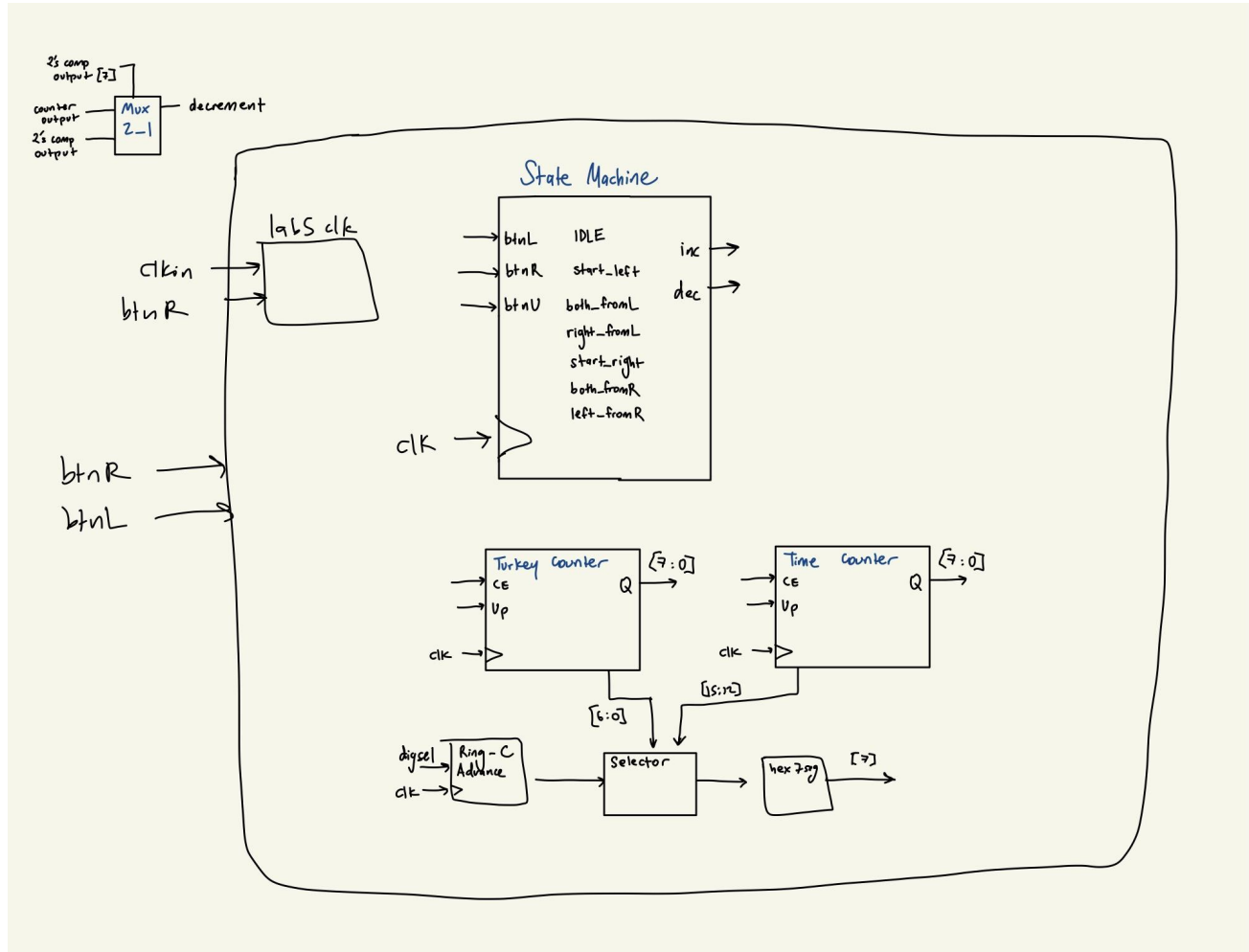

State Machine:

I have a state diagram with 7 states starting from Idle which can either go in the sequence of Right, Both, Left from right to increment a point, or Left, Both, Right from Left to decrement a point. In detail, the way the state machine works is that you start from Idle state where the *btnL* and *btnR* buttons are set high for me in order to keep LED15 and LED9 on by default. From there, if the turkey comes from the right, which means only the buttonL is high, it will go into the right state. From the right state it can go back to idle state, or the turkey can go into the both state where none of the two buttons are high because both sensors can sense the turkey being in the middle. Then comes the left state where only the left button senses the turkey which means the turkey successfully crossed the full path and we can go back to idle state and increment our turkey counter by one. Another route the turkey can take is to start from the Left State but the only difference is that if the turkey successfully passes the path from left to right, we decrement the counter by 1.

State Machine Equations:

$$D0 = (Q4 * (\sim btnL \& \sim btnR)) + (Q3 * (\sim btnL \& \sim btnR)) + (Q6 * (\sim btnL \& \sim btnR)) + (Q1 * (\sim btnL \& \sim btnR)) + (Q0 * (\sim btnL \& \sim btnR))$$

$$D1 = (Q0 * (\sim btnL \& btnR)) + (Q1 * (\sim btnL \& btnR)) + (Q2 * (\sim btnL \& btnR))$$

$$D2 = (Q3 * (btnL \& btnR)) + (Q1 * (btnL \& btnR)) + (Q2 * (btnL \& btnR))$$


$$D3 = (Q3 * (btnL \& \sim btnR)) + (Q2 * (btnL \& \sim btnR))$$

$$D4 = (Q0 * (btnL \& \sim btnR)) + (Q4 * (btnL \& \sim btnR)) + (Q5 * (btnL \& \sim btnR))$$

$$D5 = (Q6 * (btnL \& btnR)) + (Q4 * (btnL \& btnR)) + (Q5 * (btnL \& btnR))$$

$$D6 = (Q6 * (\sim btnL \& btnR)) + (Q5 * (\sim btnL \& btnR))$$

State Machine Diagram:

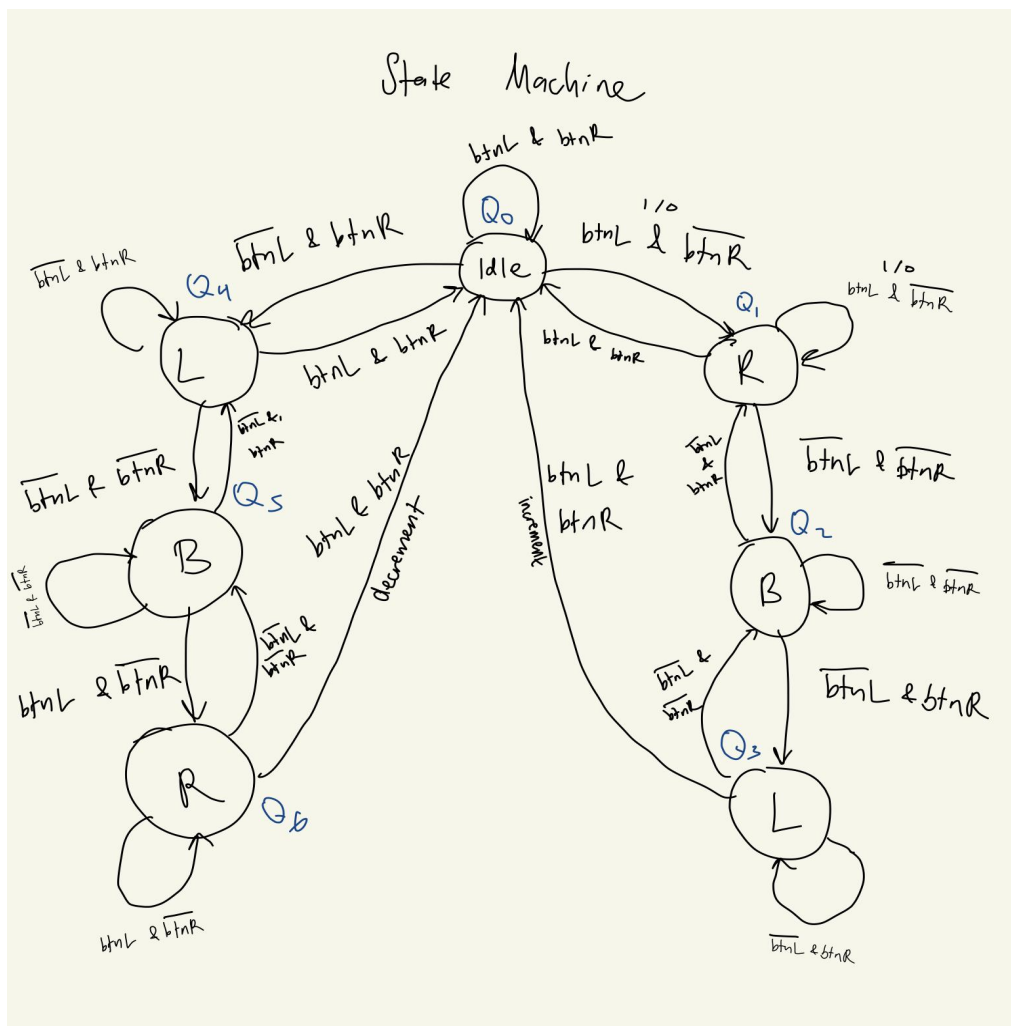

Turkey Counter:

The turkey counter is an 8 bit counter that keeps track of the turkey's movement. It can either go up or down depending on whether the turkey moves from left to right or right to left. In order to decrement into the negatives we had to implement 2's complement logic in our code to make sure that the numbers decrease as binary 0, -1, -2, -3, etc.

Time Counter:


The time counter is also an 8-bit counter that tracks the time from when one of the sensors detects a turkey. The timer only resets once both buttonL and buttonR go back to high, which means that none of the sensors detect a turkey.

Results:


Testing and Simulation:

To debug and test my code, I built a simulation for my top module and for my state machine to avoid small errors that may take a while to debug.

Simulation for Top Module:

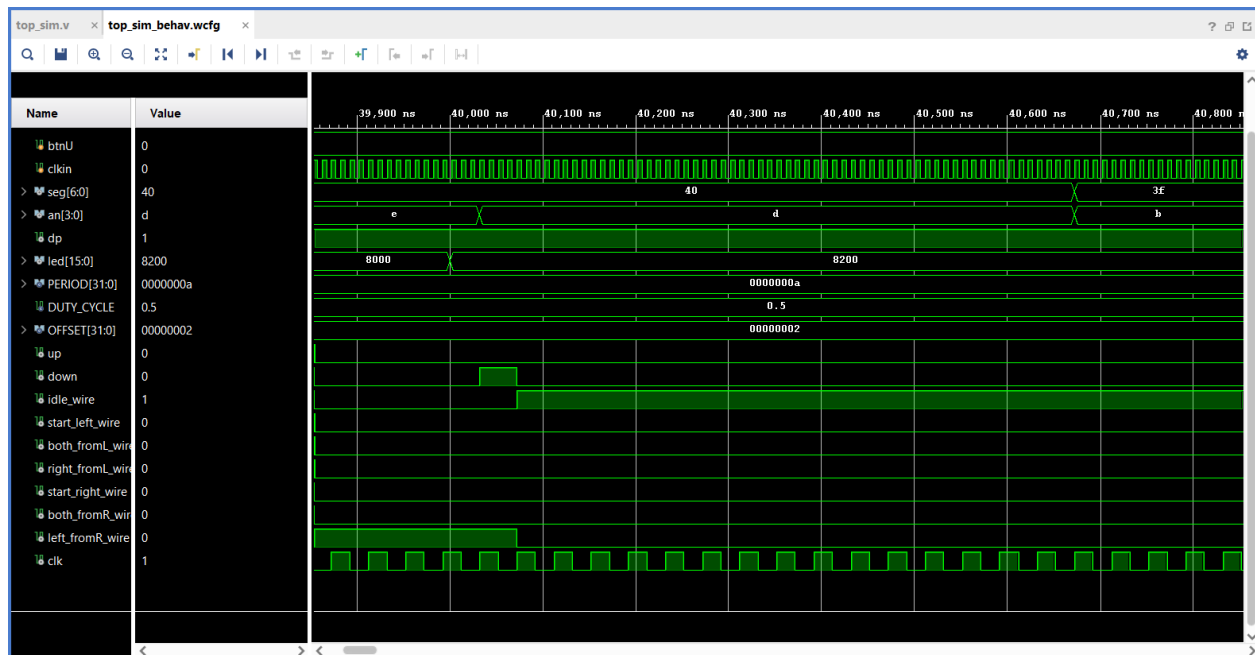

Simulation for State Machine:

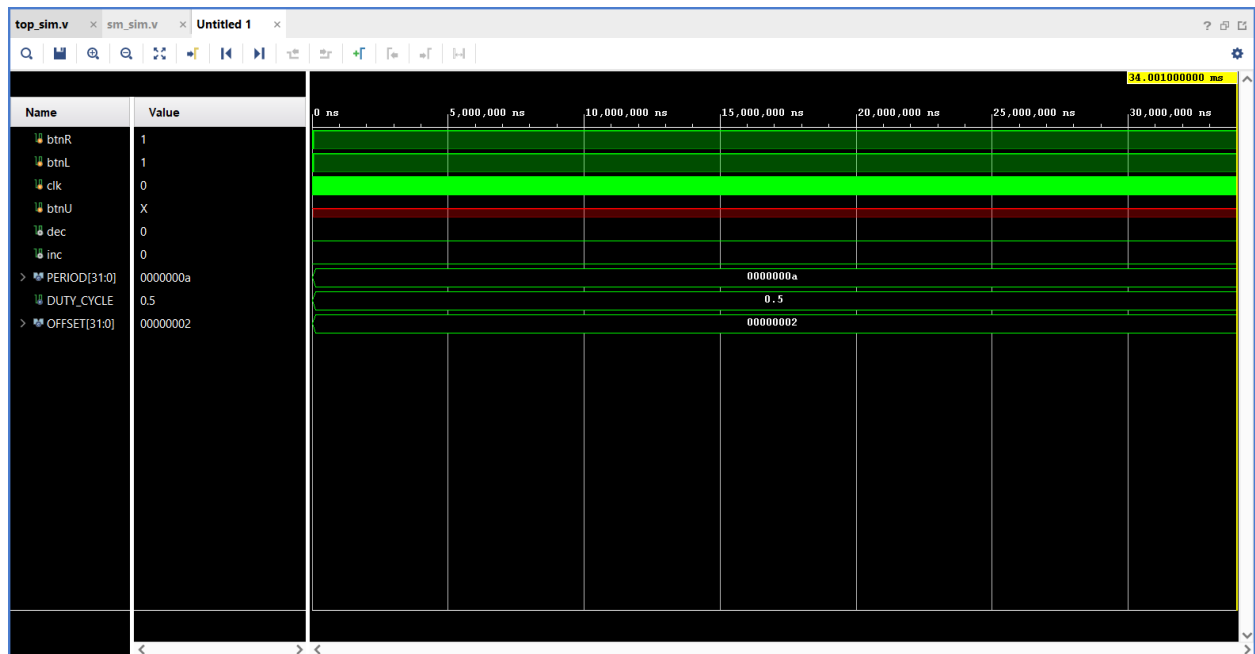

This is an example of my state machine before I fixed my btnU reset button.

Conclusion:

In conclusion, this game was created to learn how to implement state machines, use two's complement to ensure we are decrementing correctly in binary form, and to learn about sensory inputs with the simulation of buttons. Overall this lab was interesting and fun to create but the only thing that was overwhelming was spending ours debugging small errors I made here and there. At some point I had to rewrite my state machine to ensure I was doing it right. I kept testing my simulations for the state machine when my problem was in my counter module. From this I learned how crucial simulations are since they can save you a lot of time

Appendix:


reset

clk

Dw

Up

enable

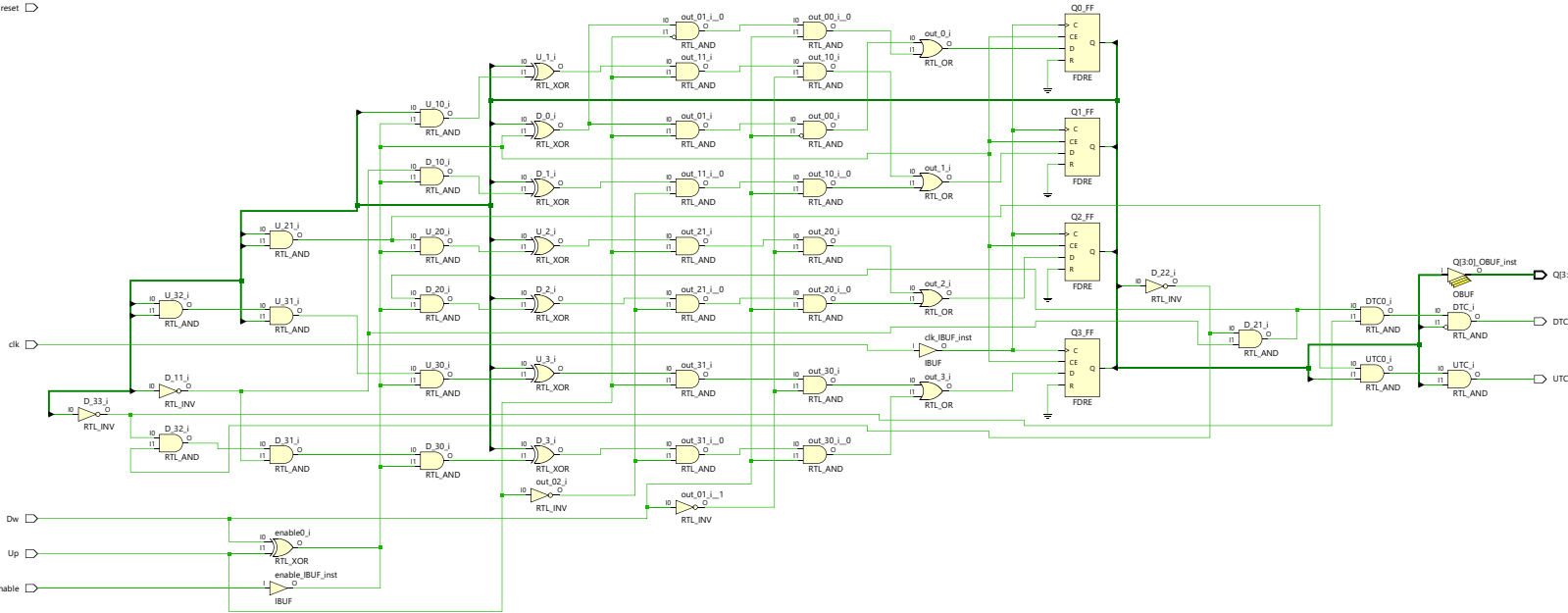

```
`timescale 1ns / 1ps
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 04/21/2022 01:43:56 PM
// Design Name:
// Module Name: countUD4L
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////

module countUD4L(
    input clk,
    input Up,
    input Dw,
    input enable,
    input reset,
    output [3:0] Q,
    output UTC,
    output DTC
);

    wire [3:0] D, U;
    wire [3:0] out;
```

```

assign UTC = Q[0] & Q[1] & Q[2] & Q[3];
assign DTC = ~Q[0] & ~Q[1] & ~Q[2] & ~Q[3];
assign enable = (Dw ^ Up);


    FDRE #(.INIT(1'b0) ) Q0_FF (.C(clk), .CE(enable), .Q(Q[0]),
.D(out[0]));
    FDRE #(.INIT(1'b0) ) Q1_FF (.C(clk), .CE(enable), .Q(Q[1]),
.D(out[1]));
    FDRE #(.INIT(1'b0) ) Q2_FF (.C(clk), .CE(enable), .Q(Q[2]),
.D(out[2]));
    FDRE #(.INIT(1'b0) ) Q3_FF (.C(clk), .CE(enable), .Q(Q[3]),
.D(out[3]));

// increment
assign U[0] = Q[0] ^ enable;
assign U[1] = Q[1] ^ (Q[0] & enable); // Q[1]
XOR Q[0]
assign U[2] = Q[2] ^ (Q[1] & Q[0] & enable); // Q[2]
XOR (Q[1] AND Q[0])
assign U[3] = Q[3] ^ (Q[2] & Q[1] & Q[0] & enable); // Q[3]
XOR (Q[1] AND Q[0] AND Q[3])

//decrement
assign D[0] = Q[0] ^ enable;
assign D[1] = Q[1] ^ (~Q[0] & enable);
// Q[1] XOR Q[0]
assign D[2] = Q[2] ^ (~Q[1] & ~Q[0] & enable);
// Q[2] XOR (Q[1] AND Q[0])
assign D[3] = Q[3] ^ (~Q[2] & ~Q[1] & ~Q[0] & enable);
// Q[3] XOR (Q[1] AND Q[0] AND Q[3])

assign out[0] = ((U[0] & Up & ~Dw) | (D[0] & ~Up & Dw));
assign out[1] = ((U[1] & Up & ~Dw) | (D[1] & ~Up & Dw));
assign out[2] = ((U[2] & Up & ~Dw) | (D[2] & ~Up & Dw));
assign out[3] = ((U[3] & Up & ~Dw) | (D[3] & ~Up & Dw));
endmodule

```
 
```
`timescale 1ns / 1ps
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 04/21/2022 01:43:56 PM
// Design Name:
// Module Name: countUD4L
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
////////////////////////////////////////////////////////////////

module countUD8L(
    input clk,
    input enable,
    input R,
    output [7:0] Q,
    output UTC,
    output DTC
);

    wire [7:0] D, U;

    assign UTC = Q[0] & Q[1] & Q[2] & Q[3] & Q[4] & Q[5] & Q[6] &
Q[7];
```

```
assign DTC = ~Q[0] & ~Q[1] & ~Q[2] & ~Q[3] & ~Q[4] & ~Q[5] &
~Q[6] & ~Q[7];
```

```
FDRE #(.INIT(1'b0) ) Q0_FF (.C(clk), .R(R), .CE(enable),
.Q(Q[0]), .D(U[0]));
```

```
FDRE #(.INIT(1'b0) ) Q1_FF (.C(clk), .R(R), .CE(enable),
.Q(Q[1]), .D(U[1]));
```

```
FDRE #(.INIT(1'b0) ) Q2_FF (.C(clk), .R(R), .CE(enable),
.Q(Q[2]), .D(U[2]));
```

```
FDRE #(.INIT(1'b0) ) Q3_FF (.C(clk), .R(R), .CE(enable),
.Q(Q[3]), .D(U[3]));
```

```
FDRE #(.INIT(1'b0) ) Q4_FF (.C(clk), .R(R), .CE(enable),
.Q(Q[4]), .D(U[4]));
```

```
FDRE #(.INIT(1'b0) ) Q5_FF (.C(clk), .R(R), .CE(enable),
.Q(Q[5]), .D(U[5]));
```

```
FDRE #(.INIT(1'b0) ) Q6_FF (.C(clk), .R(R), .CE(enable),
.Q(Q[6]), .D(U[6]));
```

```
FDRE #(.INIT(1'b0) ) Q7_FF (.C(clk), .R(R), .CE(enable),
.Q(Q[7]), .D(U[7]));
```

```
// increment
```

```
assign U[0] = Q[0] ^ enable;
```

```
assign U[1] = Q[1] ^ (Q[0] & enable); // Q[1]
```

```
XOR Q[0]
```

```
assign U[2] = Q[2] ^ (Q[1] & Q[0] & enable); // Q[2]
```

```
XOR (Q[1] AND Q[0])
```

```
assign U[3] = Q[3] ^ (Q[2] & Q[1] & Q[0] & enable); // Q[3]
```

```
XOR (Q[1] AND Q[0] AND Q[3])
```

```
assign U[4] = Q[4] ^ (Q[3] & Q[2] & Q[1] & Q[0] & enable);
```

```
assign U[5] = Q[5] ^ (Q[4] & Q[3] & Q[2] & Q[1] & Q[0] &
enable);
```


```
assign U[6] = Q[6] ^ (Q[5] & Q[4] & Q[3] & Q[2] & Q[1] & Q[0] &
enable);
```

```
assign U[7] = Q[7] ^ (Q[6] & Q[5] & Q[4] & Q[3] & Q[2] & Q[1] &
Q[0] & enable);
```

```
//decrement
```

```
assign D[0] = Q[0] ^ enable;
assign D[1] = Q[1] ^ (~Q[0] & enable);
// Q[1] XOR Q[0]
assign D[2] = Q[2] ^ (~Q[1] & ~Q[0] & enable);
// Q[2] XOR (Q[1] AND Q[0])
assign D[3] = Q[3] ^ (~Q[2] & ~Q[1] & ~Q[0] & enable);
// Q[3] XOR (Q[1] AND Q[0] AND Q[3])
assign D[4] = Q[4] ^ (~Q[3] & ~Q[2] & ~Q[1] & ~Q[0] & enable);
assign D[5] = Q[5] ^ (~Q[4] & ~Q[3] & ~Q[2] & ~Q[1] & ~Q[0] &
enable);
    assign D[6] = Q[6] ^ (~Q[5] & ~Q[4] & ~Q[3] & ~Q[2] & ~Q[1] &
~Q[0] & enable);
    assign D[7] = Q[7] ^ (~Q[6] & ~Q[5] & ~Q[4] & ~Q[3] & ~Q[2] &
~Q[1] & ~Q[0] & enable);

endmodule
```

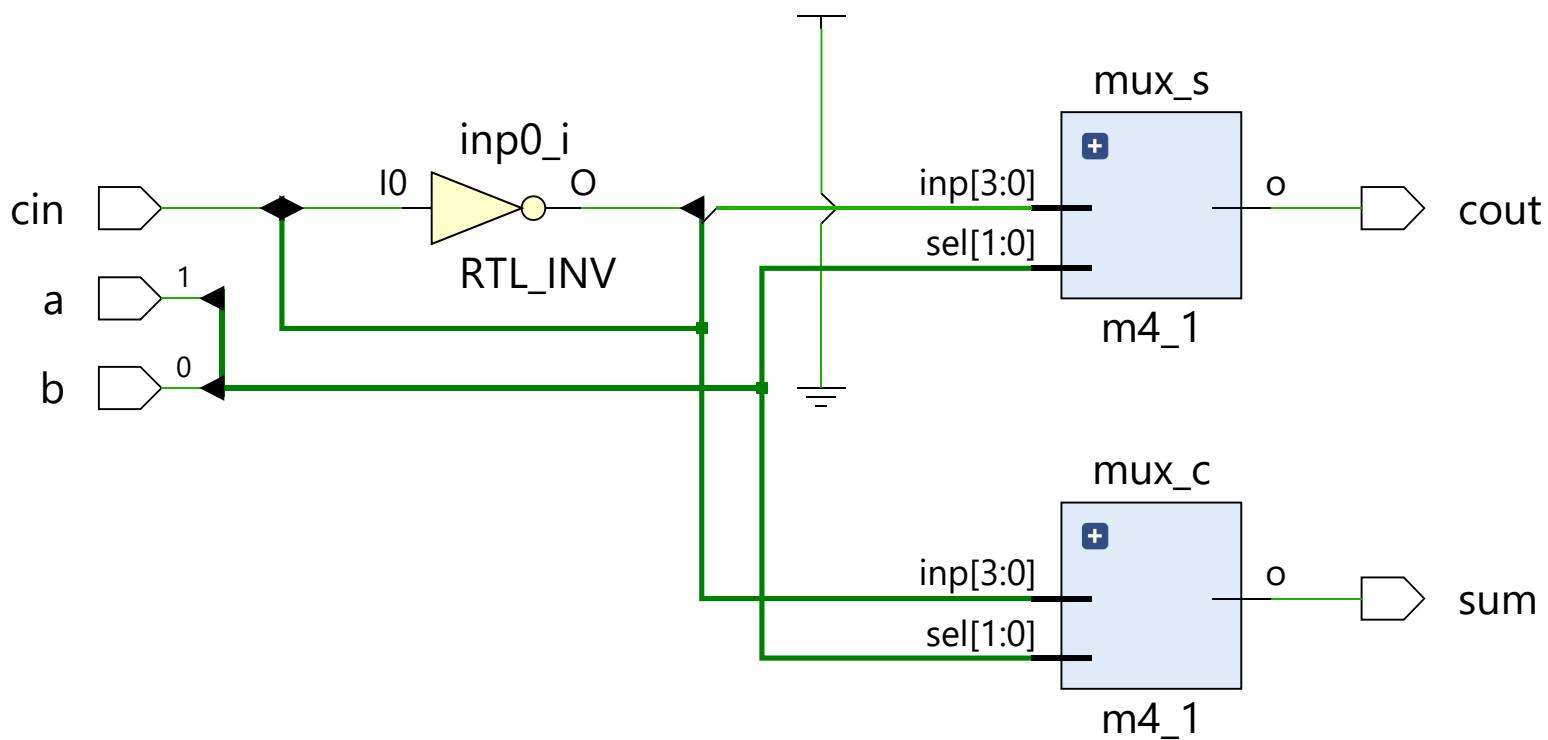

```


\timescale 1ns / 1ps
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 04/12/2022 01:44:49 PM
// Design Name:
// Module Name: full_adder
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
////////////////////////////////////////////////////////////////

module full_adder(
    input a,
    input b,
    input cin,
    output cout,
    output sum
);

    m4_1 mux_s (.inp({1'b1,cin,cin,1'b0}), .sel({a,b}), .o(cout));
    m4_1 mux_c (.inp({cin, ~cin, ~cin, cin}), .sel({a, b}),
.o(sum));

endmodule

```

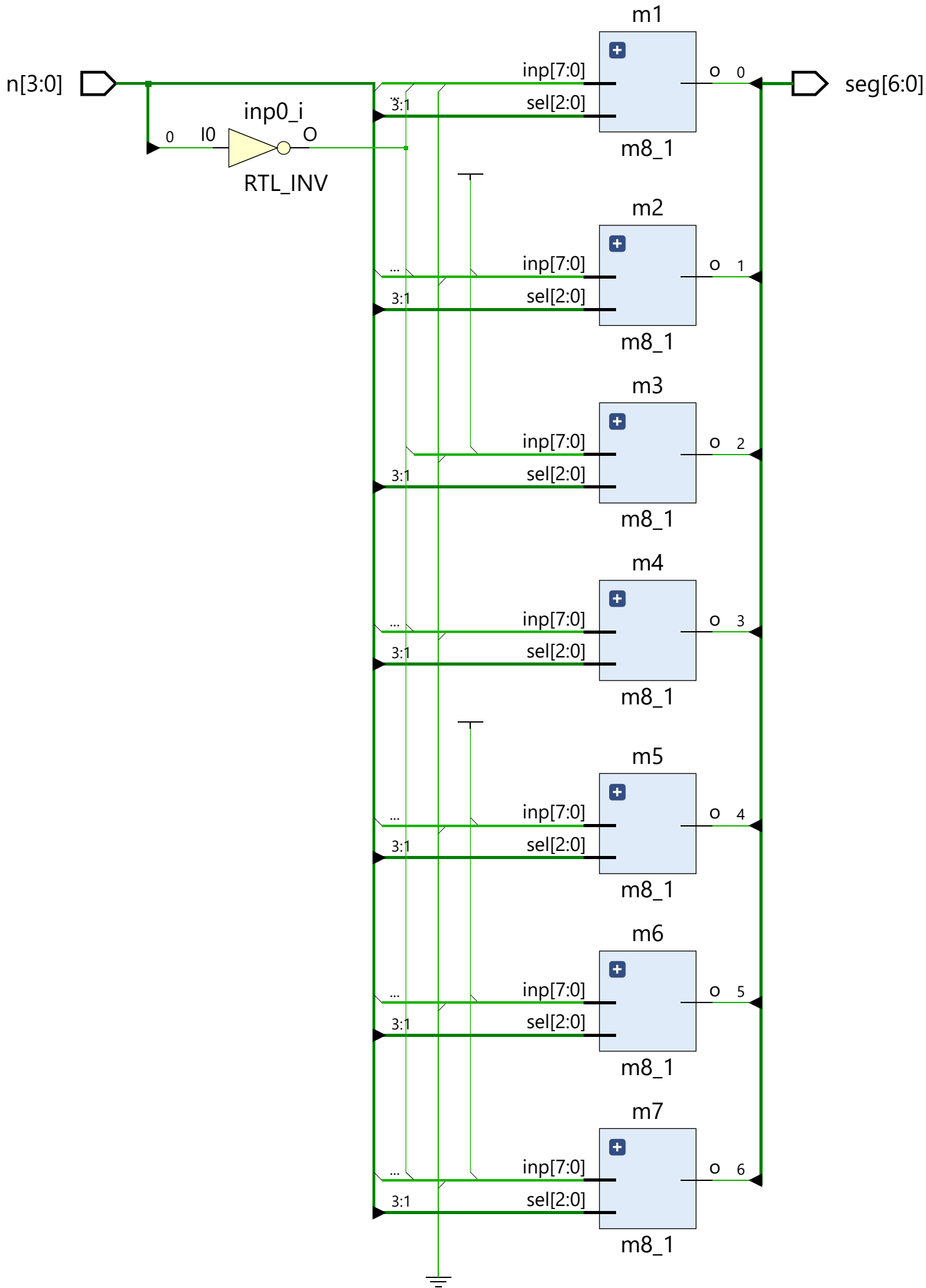

```

\timescale 1ns / 1ps
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 05/03/2022 02:36:09 PM
// Design Name:
// Module Name: hex7seg
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
////////////////////////////////////////////////////////////////

module hex7seg(
input [3:0] n,
    output [6:0] seg
);


    m8_1 m1 (.inp({1'b0, n[0], n[0], 1'b0, 1'b0, ~n[0], 1'b0,
n[0]}), .sel({n[3], n[2], n[1]}), .o(seg[0]));
    m8_1 m2 (.inp({1'b1, ~n[0], n[0], 1'b0, ~n[0], n[0], 1'b0,
1'b0}), .sel({n[3], n[2], n[1]}), .o(seg[1]));
    m8_1 m3 (.inp({1'b1, ~n[0], 1'b0, 1'b0, 1'b0, 1'b0, ~n[0],
1'b0}), .sel({n[3], n[2], n[1]}), .o(seg[2]));
    m8_1 m4 (.inp({n[0], 1'b0, ~n[0], n[0], n[0], ~n[0], 1'b0,
n[0]}), .sel({n[3], n[2], n[1]}), .o(seg[3]));

```



```
    m8_1 m5 (.inp({1'b0, 1'b0, 1'b0, n[0], n[0], 1'b1, n[0],
n[0]}), .sel({n[3], n[2], n[1]}), .o(seg[4]));
    m8_1 m6 (.inp({1'b0, n[0], 1'b0, 1'b0, n[0], 1'b0, 1'b1,
n[0]}), .sel({n[3], n[2], n[1]}), .o(seg[5]));
    m8_1 m7 (.inp({1'b0, ~n[0], 1'b0, 1'b0, n[0], 1'b0, 1'b0,
1'b1}), .sel({n[3], n[2], n[1]}), .o(seg[6]));
```

```
endmodule
```

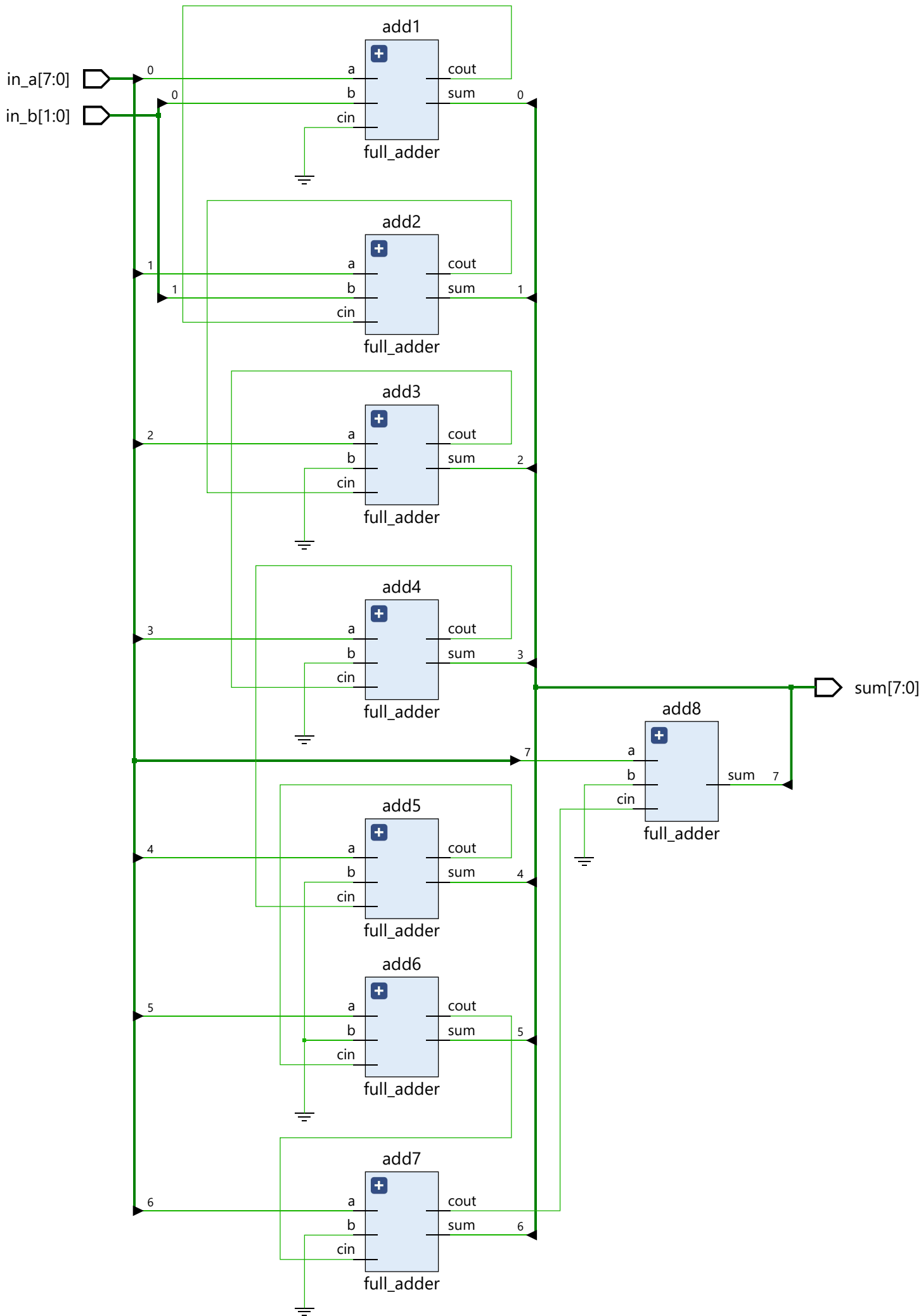

```
`timescale 1ns / 1ps
/////////////////////////////////
/////////////////////////////////
//
// Company:
// Engineer:
//
// Create Date: 04/12/2022 01:59:04 PM
// Design Name:
// Module Name: incrementer
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
/////////////////////////////////
/////////////////////////////////
```

```
module incrementer(
    input [7:0] in_a,
    input [1:0] in_b,
    output [7:0] sum
);

    wire [7:0] w;

    full_adder add1 (.a(in_a[0]), .b(in_b[0]), .cin(1'b0),
.cout(w[0]), .sum(sum[0]));
    full_adder add2 (.a(in_a[1]), .b(in_b[1]), .cin(w[0]),
.cout(w[1]), .sum(sum[1]));
```

```
    full_adder add3 (.a(in_a[2]), .b(1'b0), .cin(w[1]),
.cout(w[2]), .sum(sum[2]));

    full_adder add4 (.a(in_a[3]), .b(1'b0), .cin(w[2]),
.cout(w[3]), .sum(sum[3]));


    full_adder add5 (.a(in_a[4]), .b(1'b0), .cin(w[3]),
.cout(w[4]), .sum(sum[4]));

    full_adder add6 (.a(in_a[5]), .b(1'b0), .cin(w[4]),
.cout(w[5]), .sum(sum[5]));

    full_adder add7 (.a(in_a[6]), .b(1'b0), .cin(w[5]),
.cout(w[6]), .sum(sum[6]));

    full_adder add8 (.a(in_a[7]), .b(1'b0), .cin(w[6]),
.cout(w[7]), .sum(sum[7]));

endmodule
```

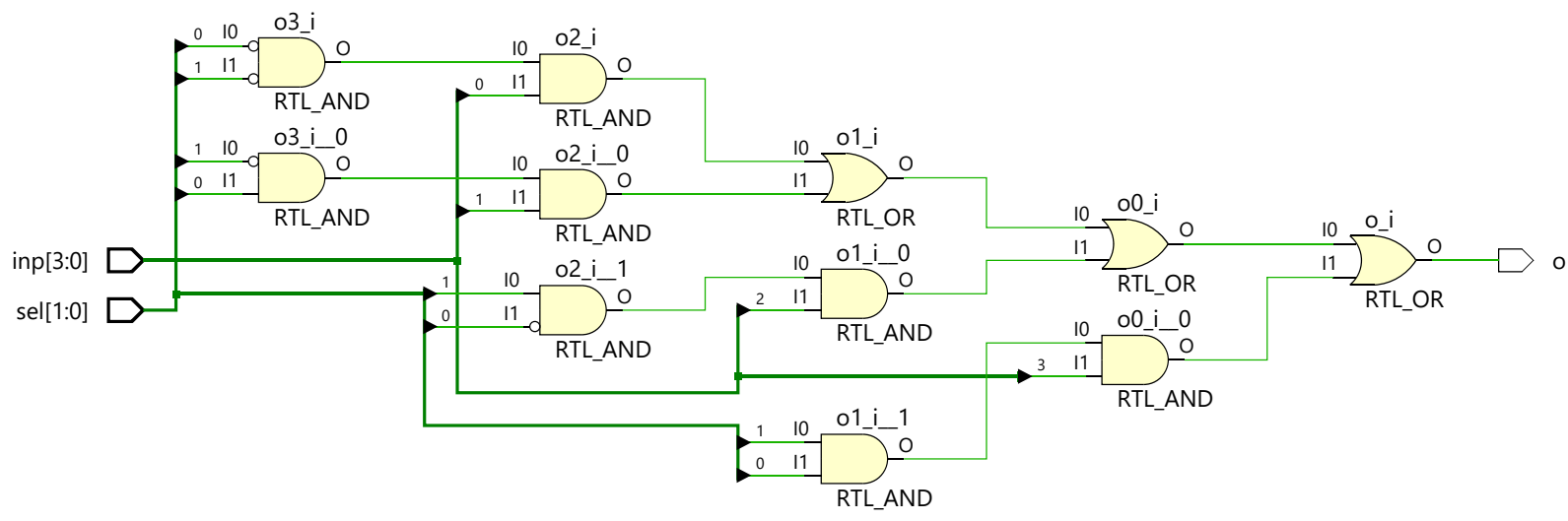


```
\timescale 1ns / 1ps
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 04/11/2022 03:00:32 PM
// Design Name:
// Module Name: m4_1
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
////////////////////////////////////////////////////////////////

module m4_1(
    input [1:0] sel,
    input [3:0] inp,
    output o
);

    assign o = ((~sel[0]&~sel[1]&inp[0]) | (~sel[1]&sel[0]&inp[1])
| (sel[1]&~sel[0]&inp[2]) | (sel[1]&sel[0]&inp[3]));


endmodule
```

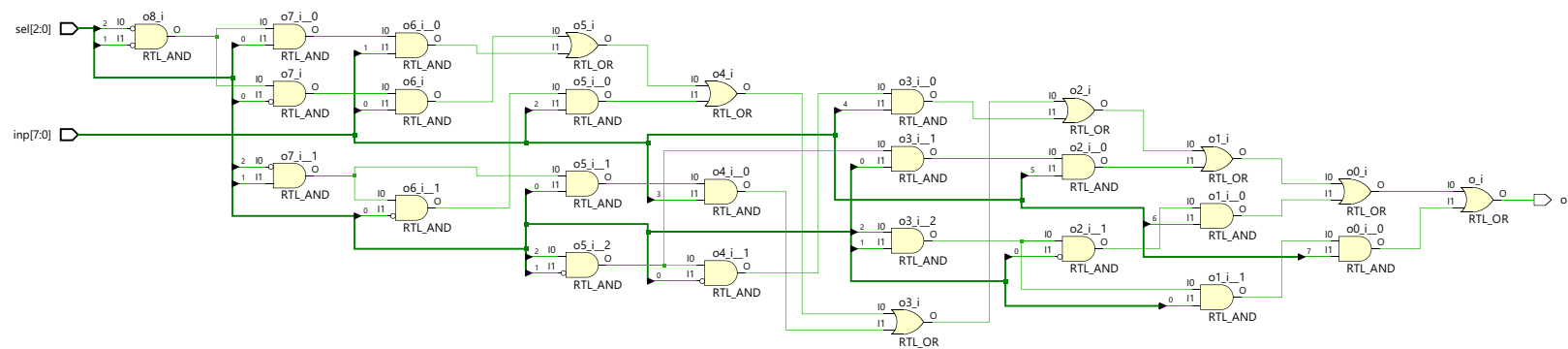

```
`timescale 1ns / 1ps
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 05/03/2022 02:39:33 PM
// Design Name:
// Module Name: m8_1
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
////////////////////////////////////////////////////////////////

module m8_1(
    input [2:0] sel,
    input [7:0] inp,
    output o
);

    assign o = ((~sel[2]&~sel[1]&~sel[0]&inp[0]) |
(~sel[2]&~sel[1]&sel[0]&inp[1]) |
    (~sel[2]&sel[1]&~sel[0]&inp[2]) |
(~sel[2]&sel[1]&sel[0]&inp[3]) | (sel[2]&~sel[1]&~sel[0]&inp[4]) |
    (sel[2]&~sel[1]&sel[0]&inp[5]) | (sel[2]&sel[1]&~sel[0]&inp[6])
| (sel[2]&sel[1]&sel[0]&inp[7]));
endmodule
```

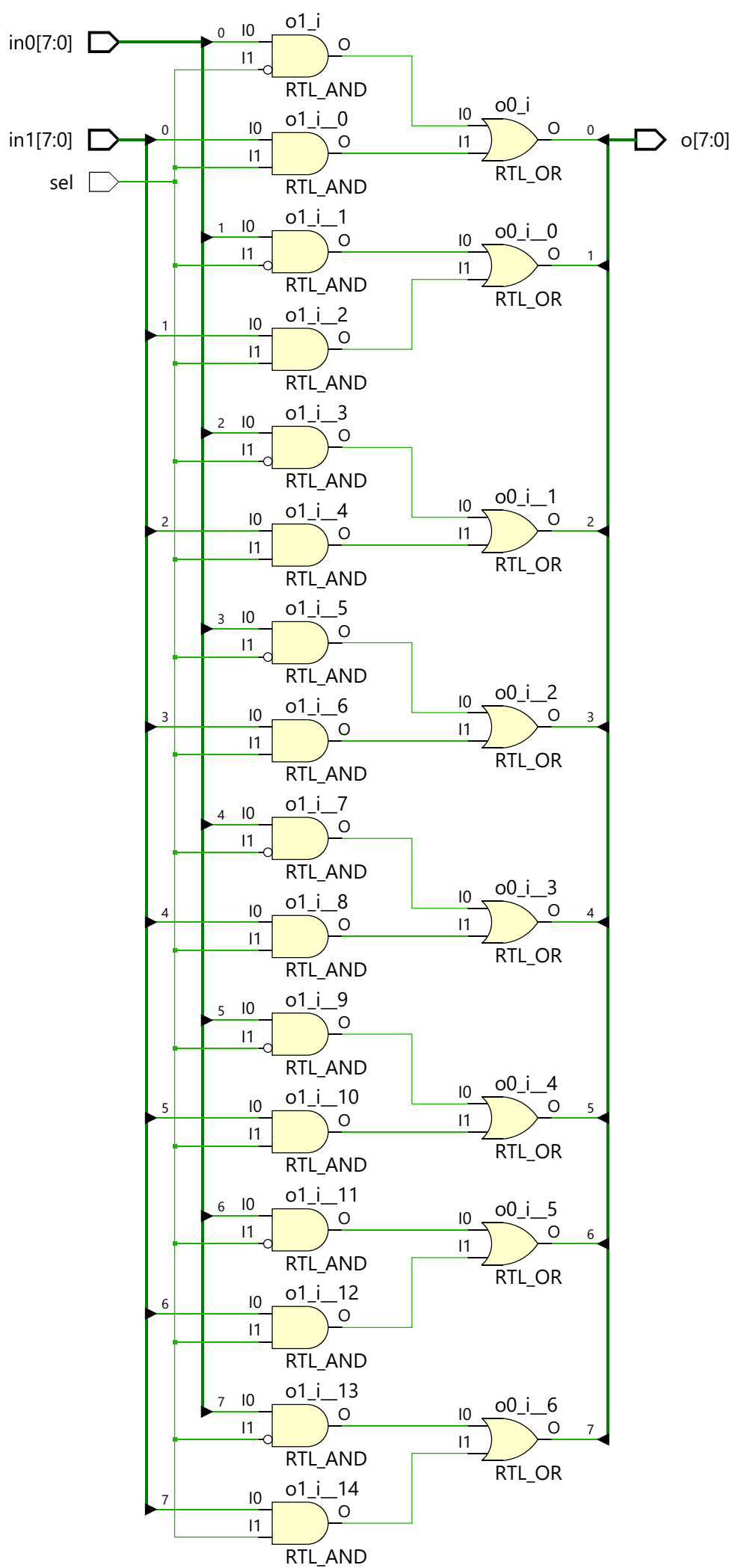
```
`timescale 1ns / 1ps
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 04/12/2022 10:08:10 PM
// Design Name:
// Module Name: m2_1x8
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
////////////////////////////////////////////////////////////////
```

```
module m2_1x8(
    input [7:0] in0,
    input [7:0] in1,
    input sel,
    output [7:0] o
);

    assign o[0] = (in0[0]&~sel) | (in1[0]&sel);
    assign o[1] = (in0[1]&~sel) | (in1[1]&sel);
    assign o[2] = (in0[2]&~sel) | (in1[2]&sel);
    assign o[3] = (in0[3]&~sel) | (in1[3]&sel);
    assign o[4] = (in0[4]&~sel) | (in1[4]&sel);
    assign o[5] = (in0[5]&~sel) | (in1[5]&sel);
```

```
    assign o[6] = (in0[6]&~sel) | (in1[6]&sel);  
    assign o[7] = (in0[7]&~sel) | (in1[7]&sel);
```

```
endmodule
```

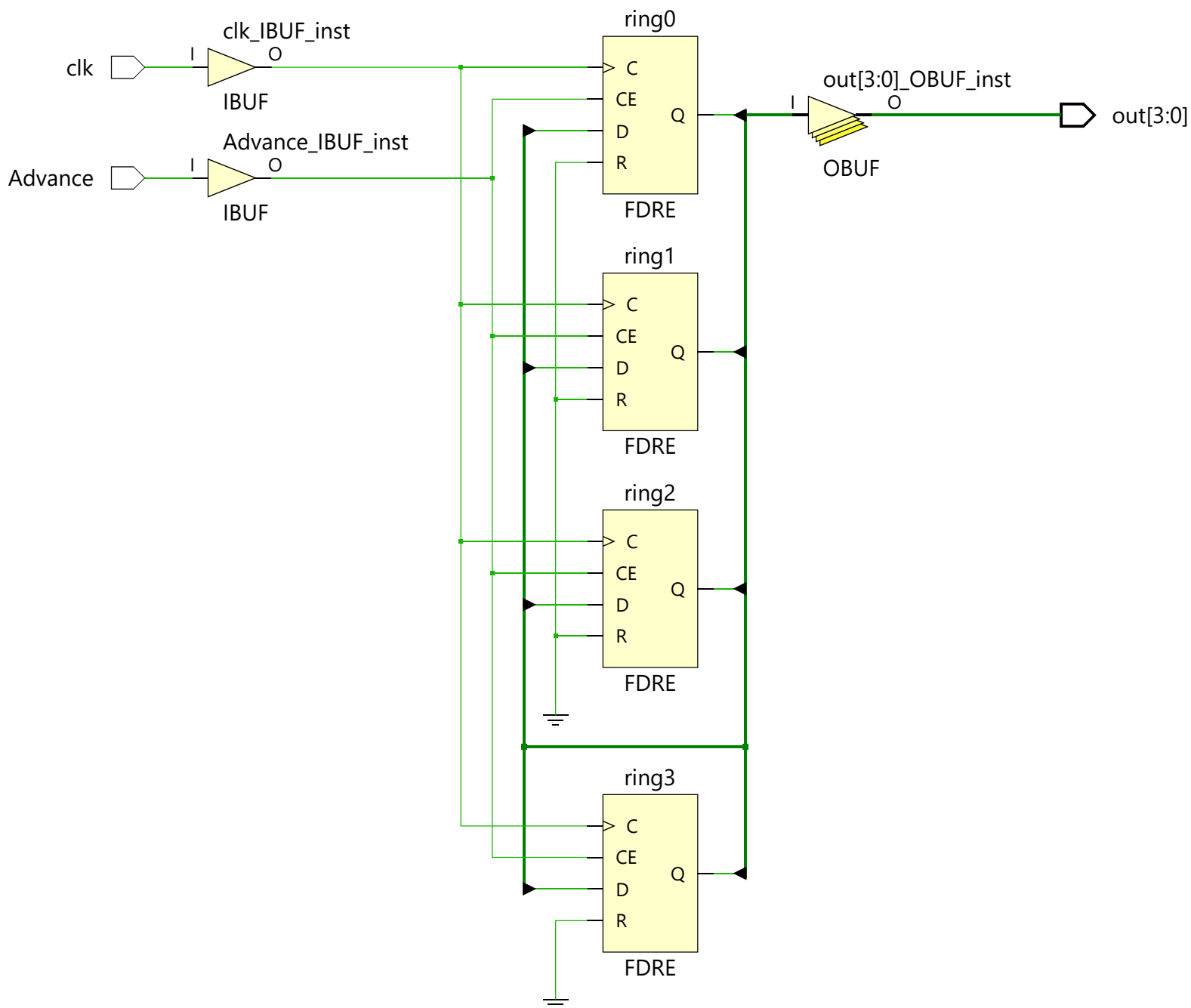

```

\timescale 1ns / 1ps
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 05/03/2022 02:42:09 PM
// Design Name:
// Module Name: ring_counter
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
////////////////////////////////////////////////////////////////


module ring_counter(
    input clk,
    input Advance,
    output [3:0] out
);

    FDRE #(.INIT(1'b1) ) ring3 (.C(clk), .R(1'b0), .CE(Advance),
.D(out[3]), .Q(out[0]));
    FDRE #(.INIT(1'b0) ) ring2 (.C(clk), .R(1'b0), .CE(Advance),
.D(out[0]), .Q(out[1]));
    FDRE #(.INIT(1'b0) ) ring1 (.C(clk), .R(1'b0), .CE(Advance),
.D(out[1]), .Q(out[2]));
    FDRE #(.INIT(1'b0) ) ring0 (.C(clk), .R(1'b0), .CE(Advance),

```

```
.D(out[2]), .Q(out[3]));
```

```
endmodule
```

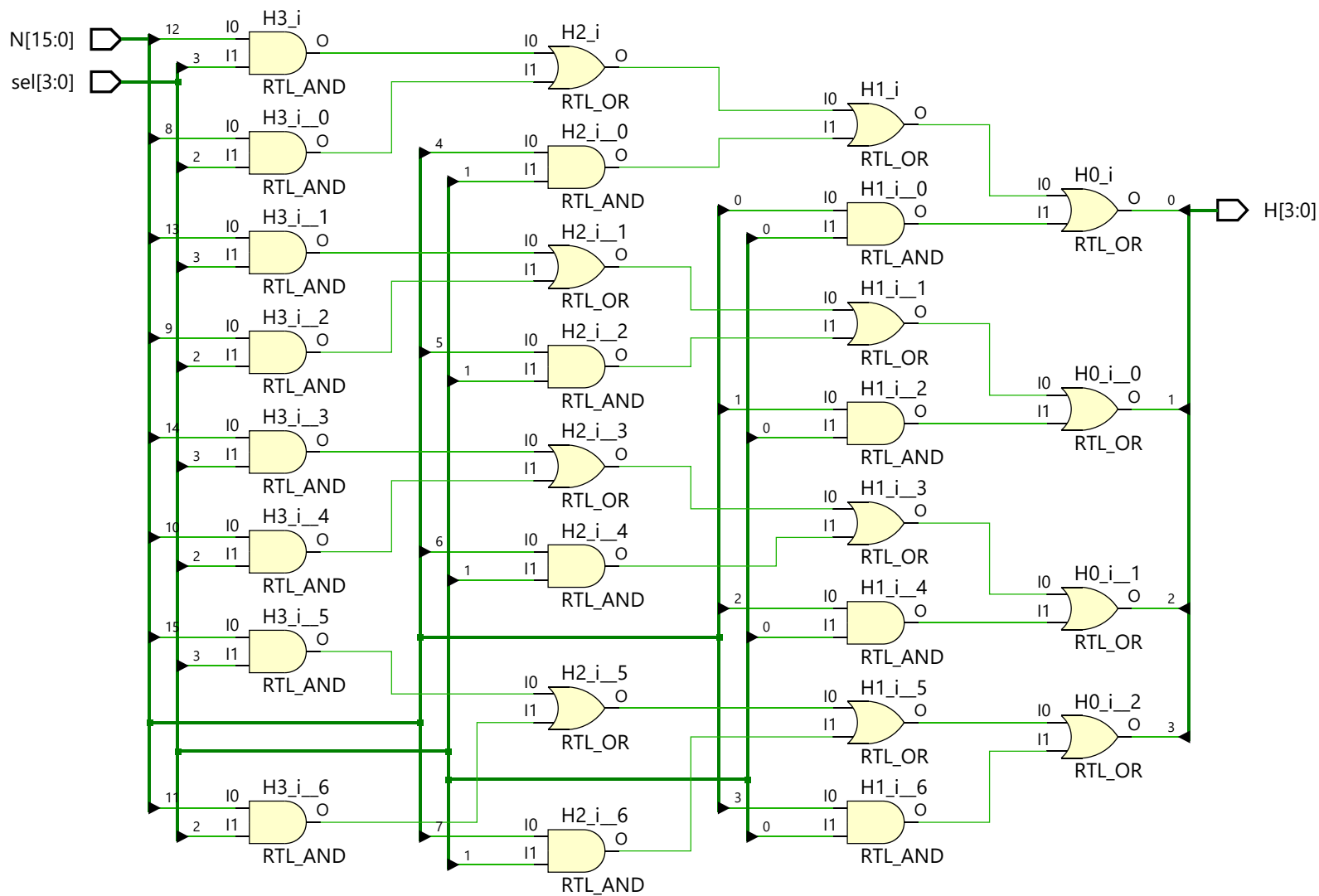

```
`timescale 1ns / 1ps
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 05/03/2022 02:37:49 PM
// Design Name:
// Module Name: selector
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
////////////////////////////////////////////////////////////////
```

```
module selector(
    input [3:0] sel,
    input [15:0] N,
    output [3:0] H
);


    //H is N[15:12] when sel=(1000)
    //H is N[11:8] when sel=(0100)
    //H is N[7:4] when sel=(0010)
    //H is N[3:0] when sel=(0001)

    assign H[0] = (N[12] & sel[3]) | (N[8] & sel[2]) | (N[4] &
sel[1]) | (N[0] & sel[0]);
```



```
        assign H[1] = (N[13] & sel[3]) | (N[9] & sel[2]) | (N[5] &
sel[1]) | (N[1] & sel[0]);
        assign H[2] = (N[14] & sel[3]) | (N[10] & sel[2]) | (N[6] &
sel[1]) | (N[2] & sel[0]);
        assign H[3] = (N[15] & sel[3]) | (N[11] & sel[2]) | (N[7] &
sel[1]) | (N[3] & sel[0]);

endmodule
```

 

```
`timescale 1ns / 1ps
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 05/10/2022 11:21:49 AM
// Design Name:
// Module Name: state_machine
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
////////////////////////////////////////////////////////////////

module state_machine(
    input clk,
    input btnL,
    input btnR,
    input btnU,
    output dec,
    output inc,
    output idle,
    output start_left,
    output both_fromL,
    output right_fromL,
    output start_right,
    output both_fromR,
```

```

output left_fromR
);

wire [6:0] D;
wire [6:0] Q;

assign idle = Q[0];
assign start_right = Q[1];
assign both_fromR = Q[2];
assign left_fromR = Q[3];
assign start_left = Q[4];
assign both_fromL = Q[5];
assign right_fromL = Q[6];

assign inc = Q[6] & D[0];
assign dec = Q[3] & D[0];


assign D[0] = (Q[4] & ~btnL & ~btnR) | (Q[3] & ~btnL & ~btnR) |
(Q[6] & ~btnL & ~btnR) | (Q[1] & ~btnL & ~btnR) | (Q[0] & ~btnL &
~btnR);
assign D[1] = (Q[0] & ~btnL & btnR) | (Q[1] & ~btnL & btnR) |
(Q[2] & ~btnL & btnR);
assign D[2] = (Q[1] & btnL & btnR) | (Q[2] & btnL & btnR) |
(Q[3] & btnL & btnR);
assign D[3] = (Q[2] & btnL & ~btnR) | (Q[3] & btnL & ~btnR);
assign D[4] = (Q[0] & btnL & ~btnR) | (Q[4] & btnL & ~btnR) |
(Q[5] & btnL & ~btnR);
assign D[5] = (Q[6] & btnL & btnR) | (Q[5] & btnL & btnR) |
(Q[4] & btnL & btnR);
assign D[6] = (Q[6] & ~btnL & btnR) | (Q[5] & ~btnL & btnR);

FDRE #(.INIT(1'b1) ) state1 (.C(clk), .CE(1'b1), .Q(Q[0]),
.D(D[0]));
FDRE #(.INIT(1'b0) ) state2 (.C(clk), .CE(1'b1), .Q(Q[1]),
.D(D[1]));
FDRE #(.INIT(1'b0) ) state3 (.C(clk), .CE(1'b1), .Q(Q[2]),
.D(D[2]));

```

```
        FDRE #(.INIT(1'b0) ) state4 (.C(clk), .CE(1'b1), .Q(Q[3]),
.D(D[3]));
        FDRE #(.INIT(1'b0) ) state5 (.C(clk), .CE(1'b1), .Q(Q[4]),
.D(D[4]));
        FDRE #(.INIT(1'b0) ) state6 (.C(clk), .CE(1'b1), .Q(Q[5]),
.D(D[5]));
        FDRE #(.INIT(1'b0) ) state7 (.C(clk), .CE(1'b1), .Q(Q[6]),
.D(D[6]));

endmodule
```

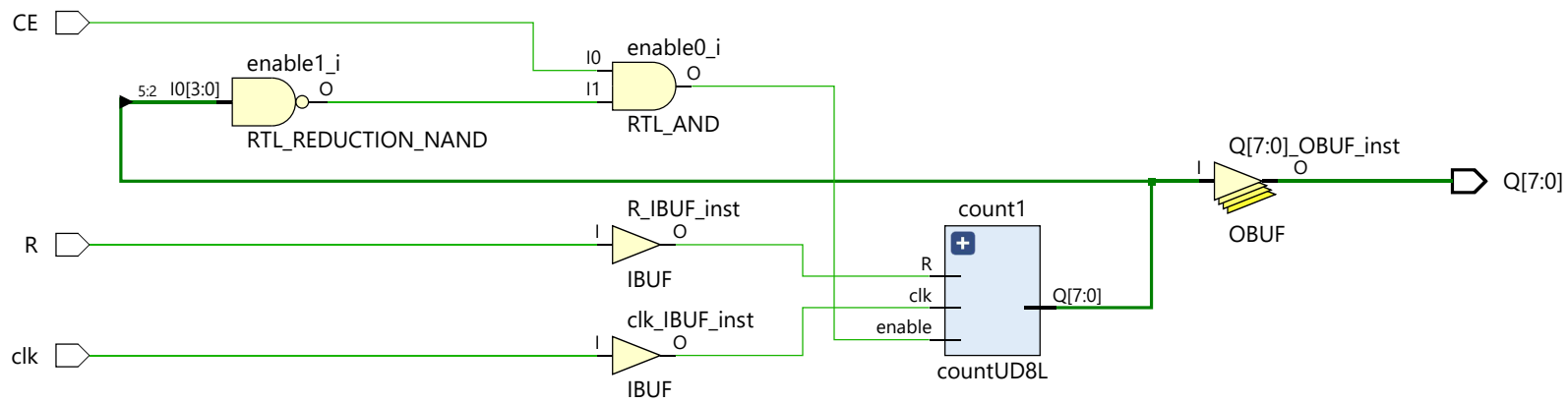

```
`timescale 1ns / 1ps
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 05/04/2022 01:40:45 PM
// Design Name:
// Module Name: time_counter
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
////////////////////////////////////////////////////////////////

module time_counter(
    input CE,
    input R,
    input clk,
    output [7:0] Q
);


    wire utc_wire;
    countUD8L count1 (.clk(clk), .enable(CE & ~&Q[5:2]), .Q(Q),
.R(R), .UTC(utc_wire));

    //wire [1:0] sel;
```

```
//assign sel[0]= CE;
//assign sel[1] = CE & utc_wire;

//countUD4L count1 (.clk(clk), .enable(CE & ~utc_wire),
.reset(R), .Q(Q), .UTC(utc_wire));
//countUD4L count2 (.clk(clk), .enable(sel[1]), .reset(R),
.Q(Q[7:4]));

endmodule
```
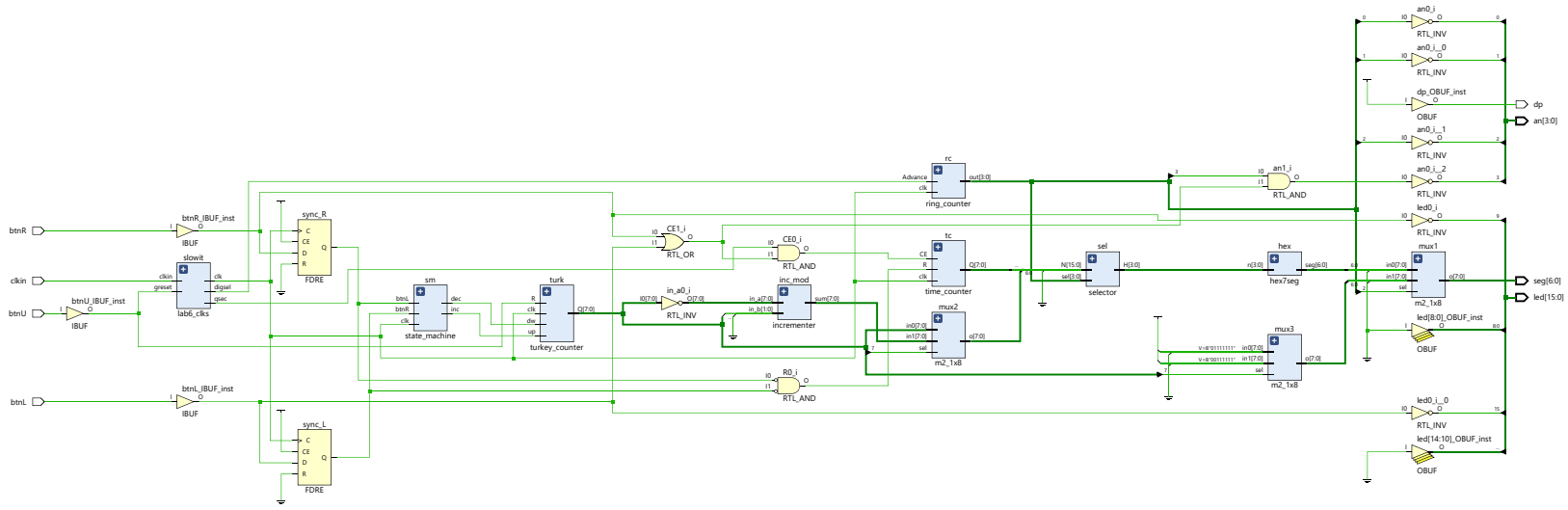
```
`timescale 1ns / 1ps
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 05/10/2022 11:22:18 AM
// Design Name:
// Module Name: top_level
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
////////////////////////////////////////////////////////////////
```

```
module top_level(
    input btnR,
    input btnL,
    input btnU,
    input clkIn,
    output [6:0] seg,
    output dp,
    output [3:0] an,
    output [15:0] led
);

//wires for lab6_clks
wire clk;
```

```

wire digsel;
wire qsec;

//wires for two's comp and neg logic
wire [6:0] twos_final;
wire [7:0] inc_wire;

wire [6:0] seg_wire;
wire [6:0] seg2_wire;

//wires for state machine outputs
wire up, down;
wire idle_wire;
wire start_left_wire;
wire both_fromL_wire;
wire right_fromL_wire;
wire start_right_wire;
wire both_fromR_wire;
wire left_fromR_wire;

//counter output buses
wire [15:0] sel_input;
wire [7:0] time_counter_wire;
wire [7:0] turkey_counter_wire;

wire btnL_wire;
wire btnR_wire;
wire [3:0] ring_wire;
wire [3:0] sel_wire;

// flip flops for sincronization of buttons
FDRE #(.INIT(1'b0) ) sync_L (.C(clk), .CE(1'b1), .Q(btnL_wire),
.D(btnL));
FDRE #(.INIT(1'b0) ) sync_R (.C(clk), .CE(1'b1), .Q(btnR_wire),
.D(btnR));

assign sel_input[15:12] = time_counter_wire[5:2];

```

```

assign sel_input[11:7] = 5'b00000;
assign sel_input[6:0] = twos_final;
assign led[9] = ~btnR;
assign led[15] = ~btnL;
assign led[8:0] = 9'b000000000;
assign led[14:10] = 5'b00000;

// muxes for negative logic
m2_1x8 mux1 (.in0(seg_wire), .in1(seg2_wire),
.sel(ring_wire[2]), .o(seg));
m2_1x8 mux3 (.in0(7'b1111111), .in1(7'b0111111),
.sel(turkey_counter_wire[7]), .o(seg2_wire));

//logic for two's complement
incrementer inc_mod (.in_a(~turkey_counter_wire),
.in_b(turkey_counter_wire[7]), .sum(inc_wire));
m2_1x8 mux2 (.in0(turkey_counter_wire), .in1(inc_wire),
.sel(turkey_counter_wire[7]), .o(twos_final));

//logic for an
assign an[0] = ~ring_wire[0];
assign an[1] = ~ring_wire[1];
assign an[2] = ~(ring_wire[2]);
assign an[3] = ~(ring_wire[3] & (btnR | btnL));
assign dp = 1'b1;

// call all functions
lab6_clks slowit (.clkin(clkin), .greset(btnU), .clk(clk),
.digsel(digsel), .qsec(qsec));

time_counter tc (.clk(clk), .R(~btnR_wire & ~btnL_wire),
.CE(qsec & (btnL | btnR)), .Q(time_counter_wire));

turkey_counter turk (.clk(clk), .up(up), .R(btnU), .dw(down),
.Q(turkey_counter_wire));

```

```
    state_machine sm (.clk(clk), .btnR(btnL_wire),  
.btnL(btnR_wire), .inc(up), .dec(down), .idle(idle_wire),  
.start_left(start_left_wire), .both_fromL(both_fromL_wire),  
.right_fromL(right_fromL_wire), .start_right(start_right_wire),  
.both_fromR(both_fromR_wire), .left_fromR(left_fromR_wire));  
  
    ring_counter rc (.Advance(digsel), .clk(clk), .out(ring_wire));  
  
    selector sel (.N(sel_input), .sel(ring_wire), .H(sel_wire));  
  
    hex7seg hex (.n(sel_wire), .seg(seg_wire));  
  
endmodule
```

```
`timescale 1ns / 1ps
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
////////////////////////////////////////////////////////////////
// Company:
// Engineer:
//
// Create Date: 05/10/2022 11:21:14 AM
// Design Name:
// Module Name: turkey_counter
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
////////////////////////////////////////////////////////////////

module turkey_counter(
    input up,
    input dw,
    input clk,
    input R,
    output [7:0] Q,
    output [7:0] D,
    output DTC,
    output UTC,
    output Z
);


    wire [1:0] utc_wire;
```

```
wire [1:0] dtc_wire;  
wire [7:0] invert;  
wire [7:0] c;
```


```
assign Z = ~(Q[7:0]);  
assign UTC = utc_wire[1] & utc_wire[0];  
assign DTC = dtc_wire[1] & dtc_wire[0];
```

```
countUD4L count1 (.clk(clk), .Up(up), .Dw(dw), .reset(R),  
.Q(Q[3:0]), .UTC(utc_wire[0]), .DTC(dtc_wire[0]));  
countUD4L count2 (.clk(clk), .Up(up & utc_wire[0] & ~dw),  
.reset(R), .Dw(dw & dtc_wire[0] & ~up), .UTC(utc_wire[1]),  
.DTC(dtc_wire[1]), .Q(Q[7:4]));
```

```
endmodule
```

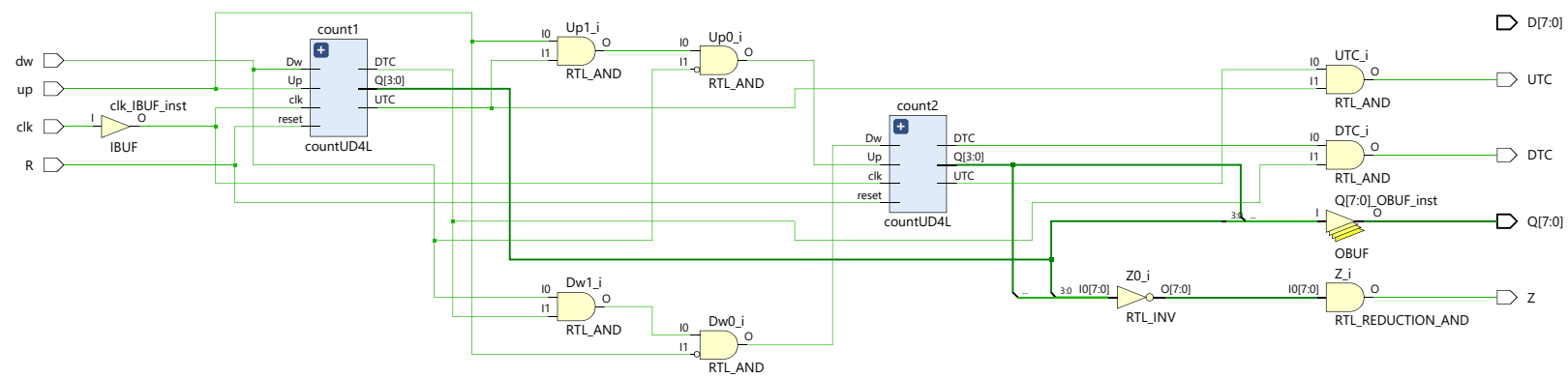

State Machine

 

State Machine Equations

$$D_0 = (Q_4 \cdot (\overline{b_{TL}} \cdot \overline{b_{TR}})) + (Q_3 \cdot (\overline{b_{TL}} \cdot \overline{b_{TR}})) + (Q_6 \cdot (\overline{b_{TL}} \cdot \overline{b_{TR}})) + (Q_1 \cdot (\overline{b_{TL}} \cdot \overline{b_{TR}})) + (Q_0 \cdot (\overline{b_{TL}} \cdot \overline{b_{TR}}))$$

$$D_1 = (Q_0 \cdot (\overline{b_{TL}} \cdot b_{TR})) + (Q_1 \cdot (\overline{b_{TL}} \cdot b_{TR})) + (Q_2 \cdot (\overline{b_{TL}} \cdot b_{TR}))$$


$$D_2 = (Q_1 \cdot (b_{tNL} \cdot b_{tNR})) + (Q_2 \cdot (b_{tNL} \cdot b_{tNR})) + (Q_3 \cdot (b_{tNL} \cdot b_{tNR}))$$

$$D_3 = \left(Q_2 \cdot (b_{tnL} \cdot \overline{b_{tnR}}) \right) + \left(Q_3 \cdot (b_{tnL} \cdot b_{tnR}) \right)$$


$$D_4 = (Q_S \cdot (\overline{btnL} \cdot btnR)) + (Q_Y \cdot (\overline{btnL} \cdot btnR))$$

$$D_S = (Q_6 \cdot (b_{tNL} \cdot b_{tNR})) + (Q_5 \cdot (b_{tNL} \cdot b_{tNR})) + (Q_4 \cdot (b_{tNL} \cdot b_{tNR}))$$


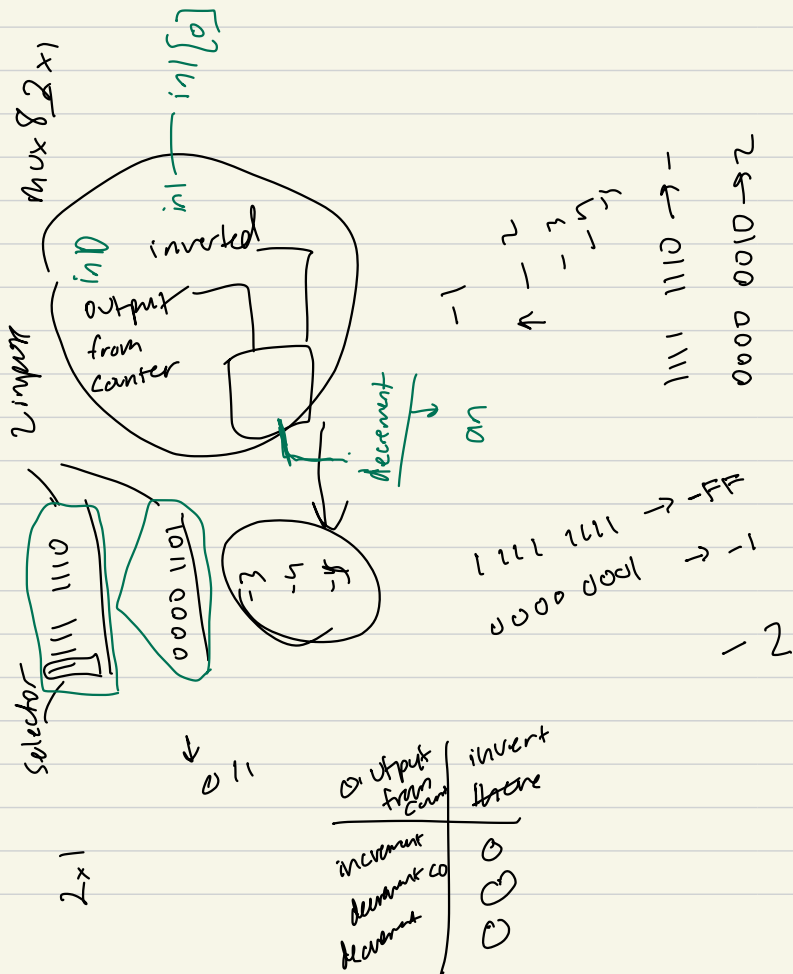
$$D_6 = (Q_0 \cdot (b_{tNL} \cdot \overline{b_{tNR}})) + (Q_6 \cdot (b_{tNL} \cdot \overline{b_{tNR}})) + (Q_5 \cdot (b_{tNL} \cdot \overline{b_{tNR}}))$$



2's complement

 

$$\begin{array}{r} \text{in0}^{\wedge} \text{in0}[7] \\ \xrightarrow{+1} \hline \text{in0} = \begin{array}{cccc} 0 & 0 & 0 & 0 \end{array} \begin{array}{cccc} 0 & 0 & 0 & 1 \end{array} \rightarrow +1 \\ \hline \begin{array}{cccc} 1 & 1 & 1 & 1 \end{array} \begin{array}{cccc} 1 & 1 & 1 & 0 \end{array} \\ + \qquad \qquad \qquad 1 \\ \hline \begin{array}{cccc} 1 & 1 & 1 & 1 \end{array} \begin{array}{cccc} 1 & 1 & 1 & 1 \end{array} \rightarrow -1 \end{array}$$

  

btnR →

btnL →

State Machine

